

Module 4.

Arithmetic

Dr. Sudhamani M J

CSE Dept.

RNSIT

Outline

- Numbers - Arithmetic Operations and Characters
- Addition and Subtraction of Signed Numbers
- Design of Fast Adders
- Multiplication of Positive Numbers
- Signed Operand Multiplication
- Fast Multiplication
- Integer Division
- Floating-point Numbers and Operations

Number, Arithmetic Operations, and Characters

- Signed Integer
- 3 major representations:

Sign and magnitude

One's complement


Two's complement

- Assumptions:

Using 4-bits 16 different values can be represented.


Roughly half are positive, half are negative

Sign and Magnitude Representation

 


High order bit is sign: 0 = positive (or zero), 1 = negative
Three low order bits is the magnitude: 0 (000) thru 7 (111)
Number range for n bits = $\pm 2^{n-1} - 1$
Two representations for 0

One's Complement Representation

 

- Subtraction implemented by addition & 1's complement
- Still two representations of 0! This causes some problems
- Some complexities in addition

Two's Complement Representation

 

- Only one representation for 0
- One more negative number than positive number

Binary, Signed-Integer Representations

B	Values represented		
$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Figure 2.1. Binary, signed-integer representations.

Addition and subtraction of binary integers

1. To add two numbers, add their n -bit representations, ignoring the carry-out signal from the MSB position. The sum will be the algebraically correct value in the 2's complement representation as long as the answer is in the range -2^{n-1} through $+2^{n-1}-1$.

2. To subtract two numbers X and Y , ie, to perform $X-Y$, form the 2's complement of Y and then add it to X , as in rule 1. the result will be algebraically correct value in the 2's complement representation as long as the answer is in the range -2^{n-1} through $+2^{n-1}-1$.

In all these 4-bit examples the answer falls in the range between -8 to +7, if it do not fall within the representable range, **then it is called arithmetic overflow.**

Examples for addition

a) 0010 (+2)

+0011 (+3)

0101 (+5)

b) 0100 (+4)

+1010 (-6)

1110 (-2)

c) 1011 (-5)

+1110 (-2)

1001 (-7)

Examples for subtraction

a) $\begin{array}{r} 1101 \quad (-3) \\ -1001 \quad (-7) \\ \hline \end{array}$ 2's complement \longrightarrow $\begin{array}{r} 1101 \\ +0111 \\ \hline 0100 \quad (+4) \end{array}$

b) $\begin{array}{r} 0010 \quad (+2) \\ -0100 \quad (+4) \\ \hline \end{array}$ 2's complement \longrightarrow $\begin{array}{r} 0010 \\ 1100 \\ \hline 1110 \quad (-2) \end{array}$

c) $\begin{array}{r} 1001 \quad (-7) \\ -1011 \quad (-5) \\ \hline \end{array}$ 2's complement \longrightarrow $\begin{array}{r} 1001 \\ 0101 \\ \hline 1110 \quad (-2) \end{array}$

Addition/subtraction of signed numbers

x_i	y_i	Carry-in C_i	Sum s_i	Carry-out C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

At the i^{th} stage:

Input:

c_i is the carry-in

Output:


s_i is the sum

c_{i+1} carry-out to $(i+1)^{st}$ state


$$s_i = \overline{x_i}y_i\overline{c_i} + \overline{x_i}y_ic_i + x_i\overline{y_i}\overline{c_i} + x_iy_ic_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_ic_i + x_ic_i + x_iy_i$$

Example:

 

Addition logic for a single stage

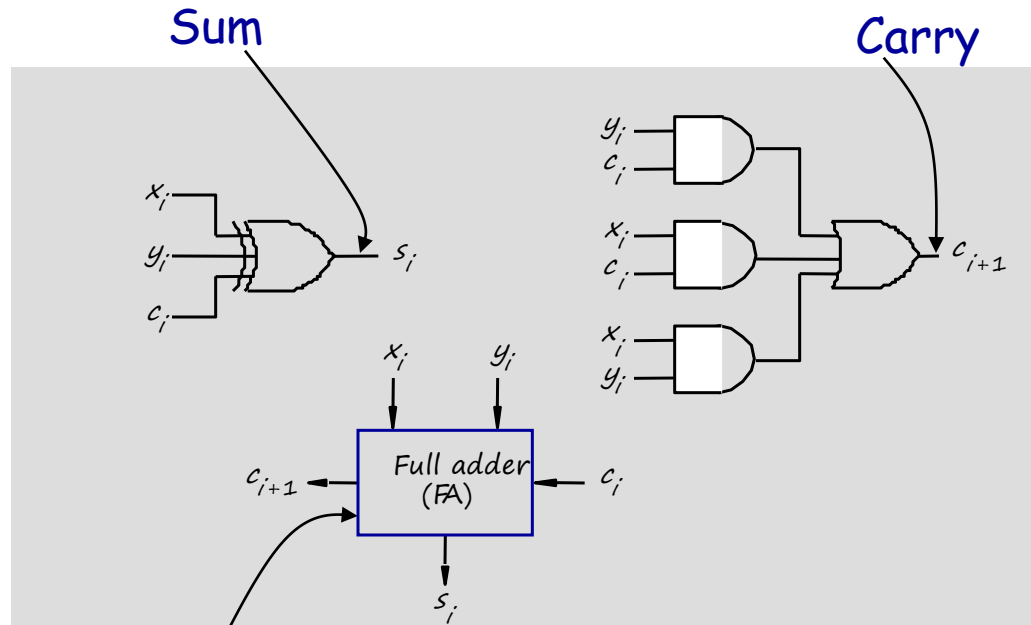


Full Adder (FA): Symbol for the complete circuit for a single stage of addition.

Full adder is combinational logical circuit that performs an addition operation on three one-bit binary numbers.

n -bit adder

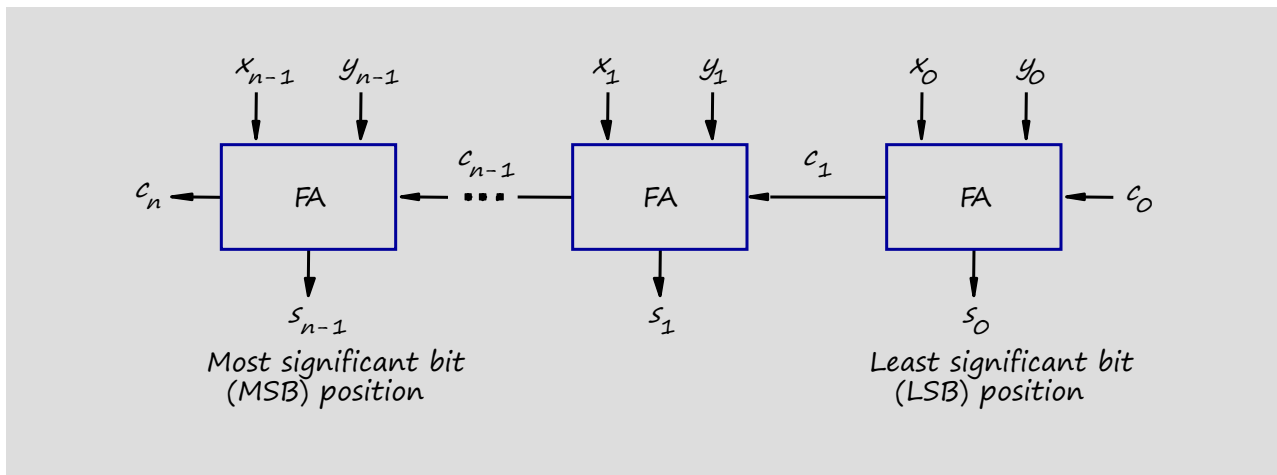
- Cascade n full adder (FA) blocks to form a n -bit adder.
- Carries propagate or ripple through this cascade, [\$n\$ -bit ripple carry adder](#).



Carry-in c_0 into the LSB position provides a convenient way to perform subtraction.

K n -bit adder

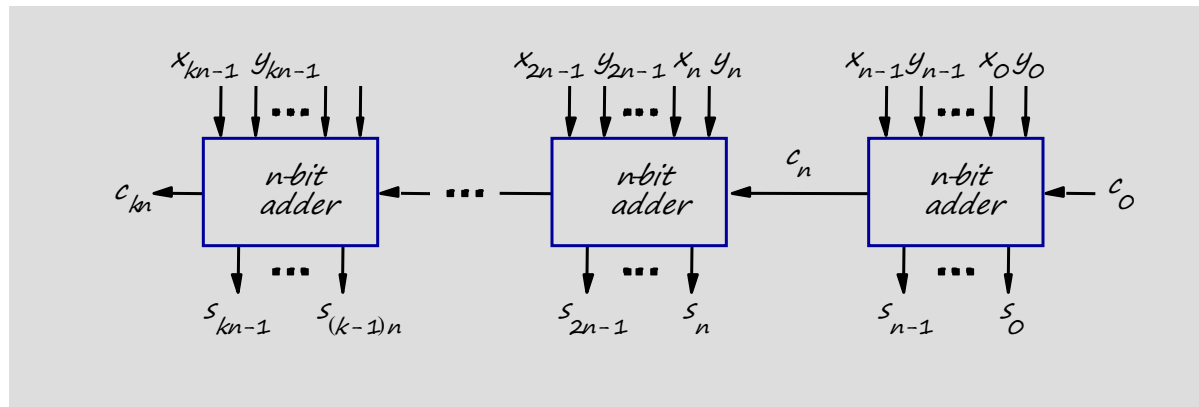
K n -bit numbers can be added by cascading k n -bit adders.



Each n -bit adder forms a block, so this is cascading of blocks.

Carries ripple or propagate through blocks, [Blocked Ripple Carry Adder](#)

n -bit adder/subtractor (contd..)

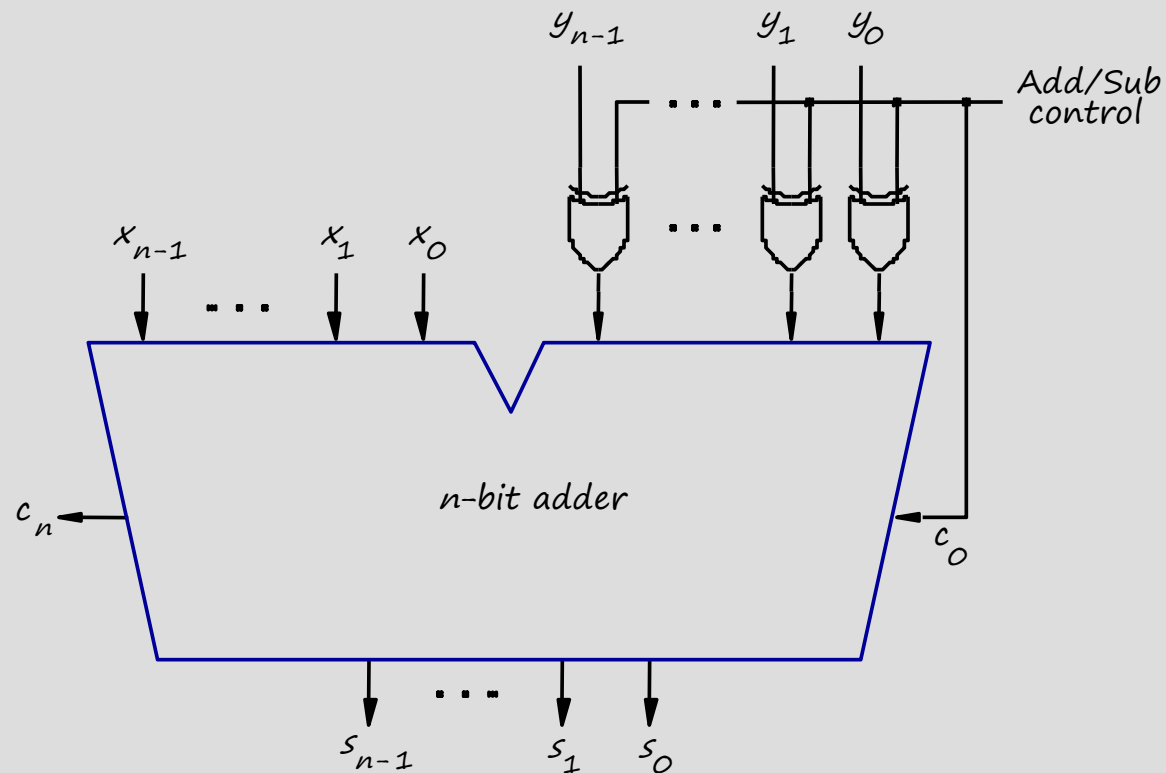


- Add/sub control = 0, addition.
- Add/sub control = 1, subtraction.

note : XOR gate
complements the bits


Finding the gate delays

 - The delay through a logic network depends on IC technology used in fabrication and on the number of gates in the paths from input to output
- Sum has 1 gate delay (XOR gate) and Carry has 2 gate delays (AND + OR gates) in FA



Gate delay in n-bit ripple carry adder

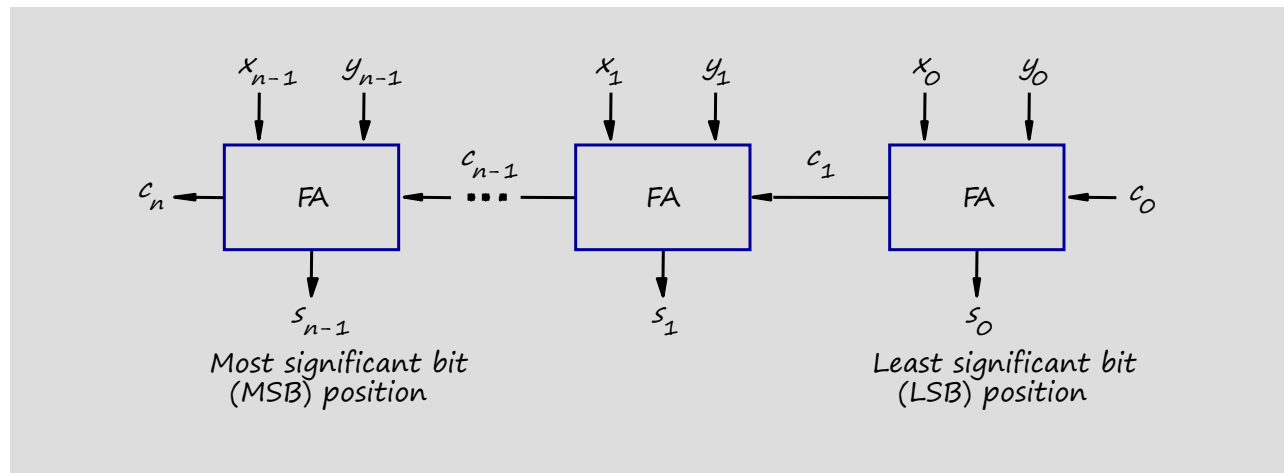- C_{n-1} is available in $2(n-1)$ gate delay
[1 for AND gate + 1 for OR gate = 2 delay * (n-1) stages $\Rightarrow 2(n-1)$]
- C_n is available in by adding 2 gate delays to $C_{n-1} \Rightarrow 2n-2+2 = 2n$ gate delays
- S_{n-1} is one XOR gate delay after C_{n-1} is obtained
- i.e $2n-2+1 = 2n-1$ gate delays



Fast addition

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- G_i is called **generate function** and P_i is called **propagate function**
- G_i and P_i are computed only from x_i and y_i and not c_i , thus they can be computed in one gate delay after X and Y are applied to the inputs of an n -bit adder.

Carry lookahead

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$



until

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- All carries can be obtained 3 gate delays after X , Y and c_0 are applied.
 - One gate delay for P_i and G_i
 - Two gate delays in the AND-OR circuit for c_{i+1}
- All sums can be obtained 1 gate delay after the carries are computed.
- Independent of n , n -bit addition requires only 4 gate delays.
- This is called Carry Lookahead adder.

Carry-lookahead adder

**4-bit
carry-lookahead
adder**

 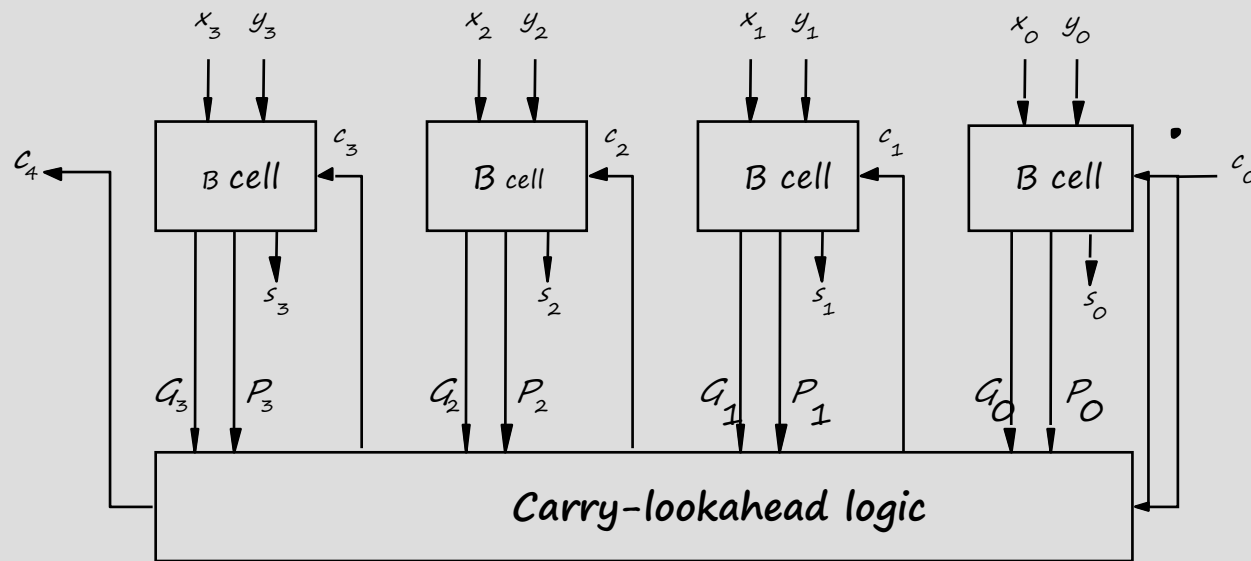

$$c_{i+1} = G_i + P_i c_i$$

where $G_i = x_i y_i$ and $P_i = x_i + y_i$

B-cell for a single stage


Carry lookahead adder (contd..)

- Performing n -bit addition in 4 gate delays independent of n is good only theoretically because of fan-in constraints.

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- Last AND gate and OR gate require a fan-in of $(n+1)$ for a n -bit adder.
 - For a 4-bit adder ($n=4$) fan-in of 5 is required.
 - Practical limit for most gates.
- In order to add operands longer than 4 bits, we can cascade 4-bit Carry-Lookahead adders. Cascade of Carry-Lookahead adders is called Blocked Carry-Lookahead adder.

16 bit Carry-Lookahead adder

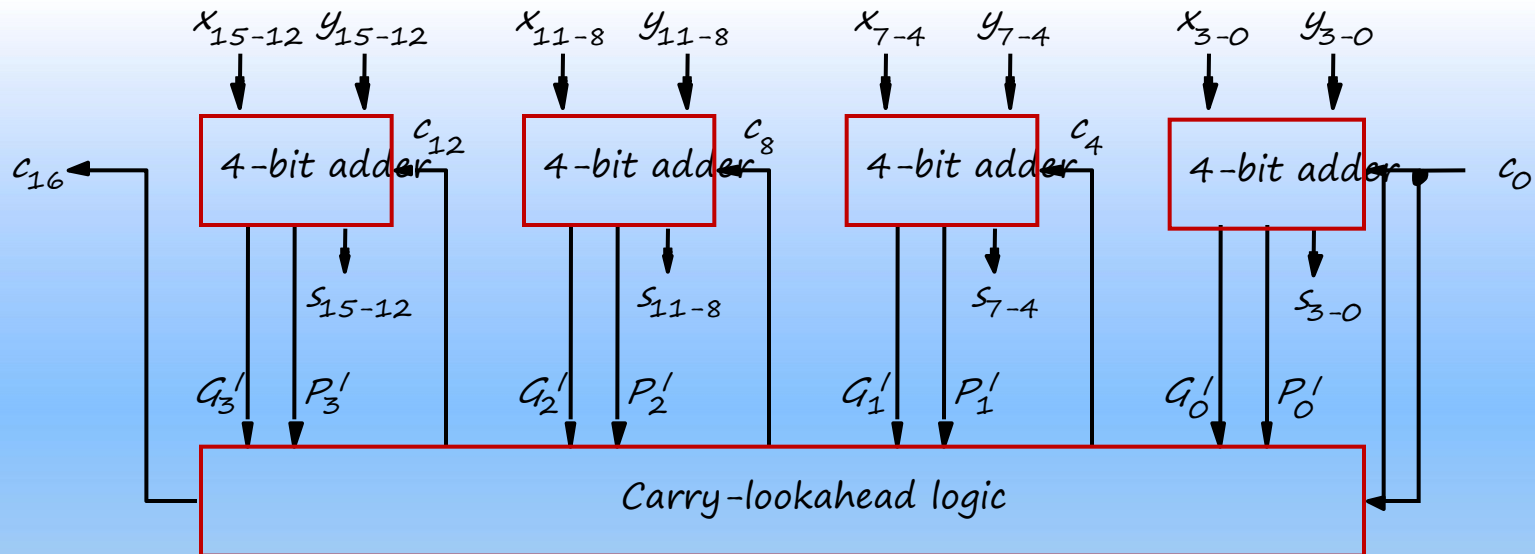

After x_i , y_i and c_0 are applied as inputs:

- G_i and P_i for each stage are available after 1 gate delay.
- P^i is available after 2 and G^i after 3 gate delays.
- All carries are available after 5 gate delays.
- c_{16} is available after 5 gate delays.
- s_{15} which depends on c_{12} is available after 8 (5+3) gate delays (Recall that for a 4-bit carry lookahead adder, the last sum bit is available 3 gate delays after all inputs are available)

Multiplication

Multiplication of unsigned numbers

1	1	0	1					(13) Multiplicand M
1	0	1	1					(11) Multiplier Q
<hr/>								
				1	1	0	1	
				1	1	0	1	
				0	0	0	0	
				1	1	0	1	
				<hr/>				
				1	0	0	0	
				1	1	1	1	
				1	0	0	0	
				1	1	1	1	(143) Product P

Product of 2 n -bit numbers is at most a $2n$ -bit number.


Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.

Multiplication of unsigned numbers (contd..)

- We added the partial products at end.
 - Alternative would be to add the partial products at each stage.
- Rules to implement multiplication are:
 - If the i^{th} bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
 - Hand over the partial product to the next stage
 - Value of the partial product at the start stage is 0.

Combinatorial array multiplier


Combinatorial array multiplier

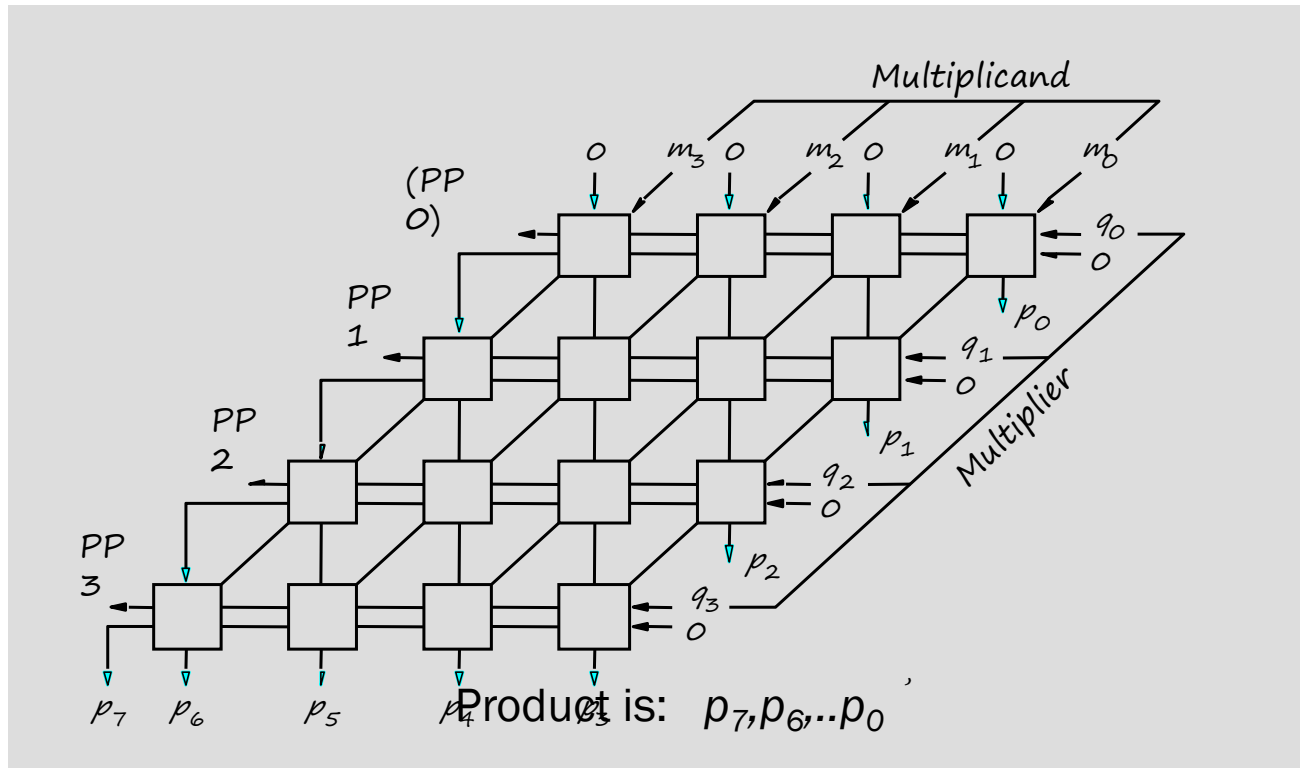

Multiplicand is shifted by displacing it through an array of adders.

Multiplication of unsigned numbers


Typical multiplication cell

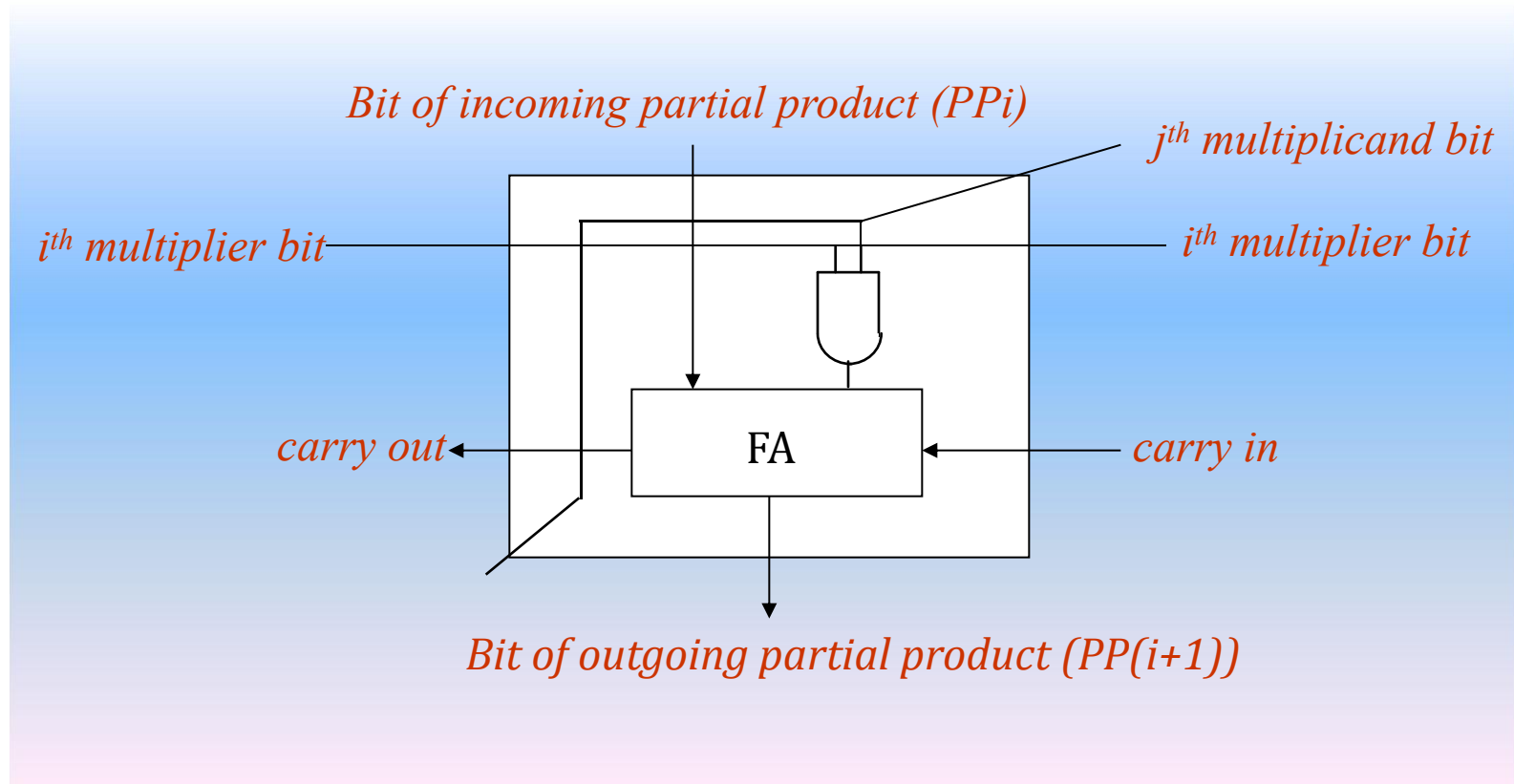

Combinatorial array multiplier (contd..)

- Combinatorial array multipliers are:
 - Extremely inefficient.
 - Have a high gate count for multiplying numbers of practical size such as 32-bit or 64-bit numbers.
 - Perform only one function, namely, unsigned integer product.
- Improve gate efficiency by using a mixture of combinatorial array techniques and sequential techniques requiring less combinational logic.

Sequential multiplication

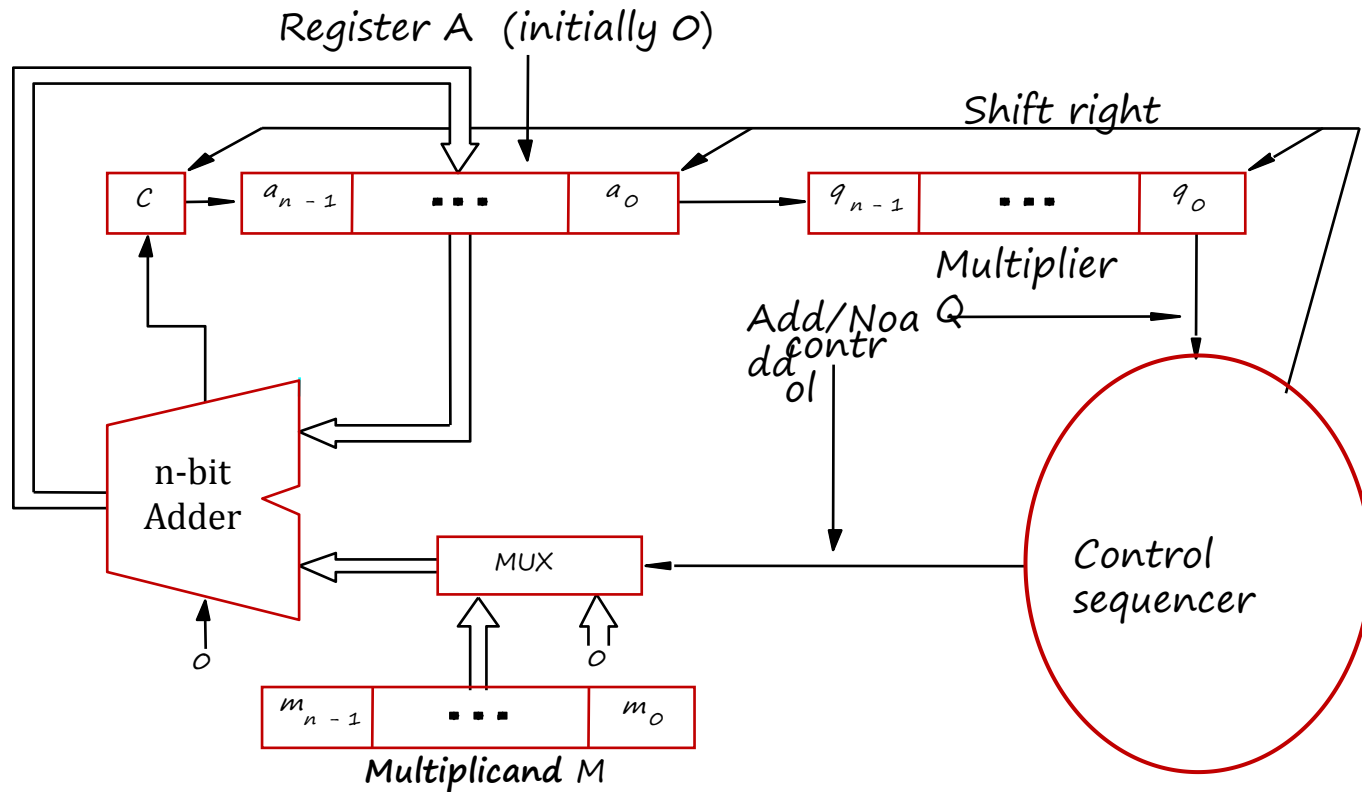

Algorithm

Load

multiplier into Register Q, Multiplicand into register M

Clear C and A

Repeat the following n-times

Step1: if Q0 is 1do the following:


1) Add M to A and keep the result in A

2) shift C, A and Q right one bit position

if Q0 is 1 goto step1; otherwise step 2

step2: if Q0 is 0, do not add M to A , just shift C,A and Q one bit position

Sequential multiplication (contd..)

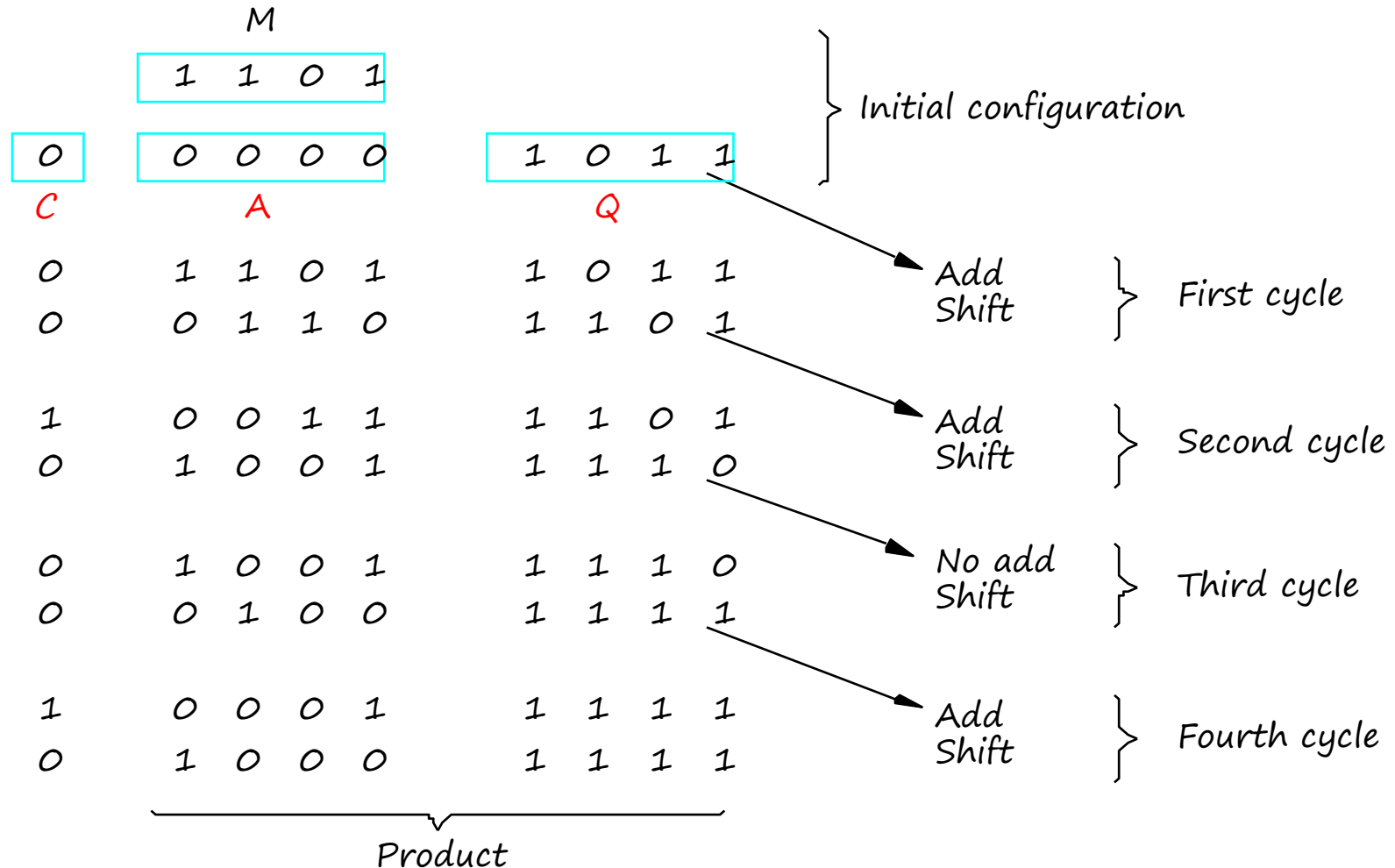

Signed Multiplication

Signed Multiplication


- Considering 2's-complement signed operands, what will happen to $(-13) \times (+11)$ if following the same method of unsigned multiplication?

Sign extension is shown in blue

					1	0	0	1	1	(-13)
					0	1	0	1	1	(+11)
					<hr/>					
1	1	1	1	1	1	0	0	1	1	
1	1	1	1	1	0	0	1	1		
0	0	0	0	0	0	0	0			
1	1	1	0	0	1	1				
0	0	0	0	0	0					
					<hr/>					
1	1	0	1	1	1	0	0	0	1	(-143)

Sign extension of negative multiplicand.

Signed Multiplication

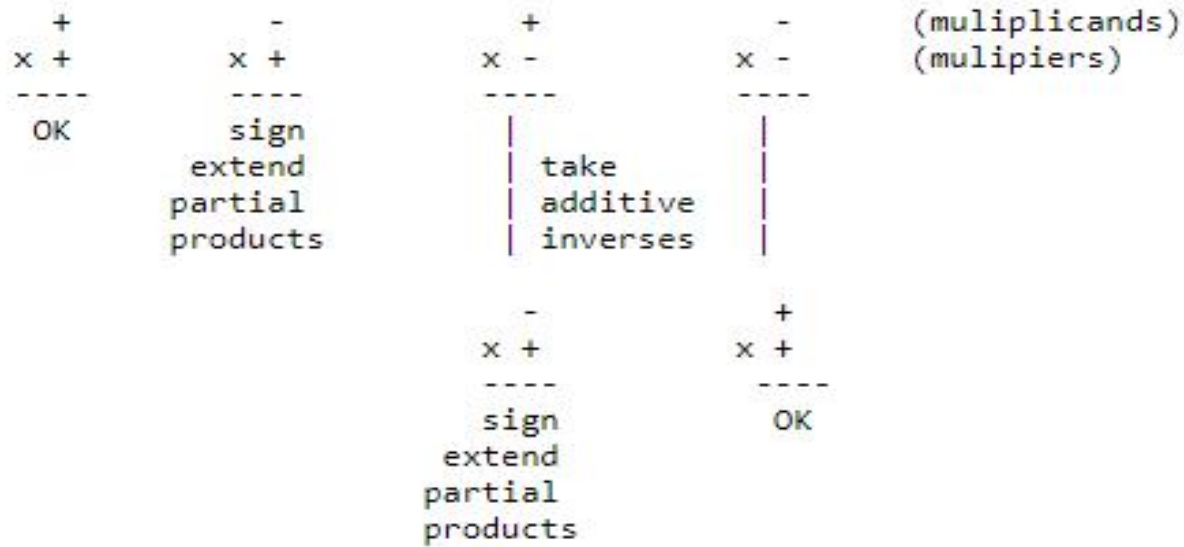

- A technique that works equally well for both negative and positive multipliers – Booth algorithm.

Booth Algorithm

- Consider in a multiplication, the multiplier is positive 0011110, how many appropriately shifted versions of the multiplicand are added in a standard procedure?

$$\begin{array}{r}
 \begin{array}{cccccccc}
 & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & & & & 0 & 0 & +1 & +1 & +1 & +1 & 0 \\
 \hline
 & & & & 0 & 0 & 0 & 0 & 0 & 0 & 0
 \end{array} \\
 \begin{array}{cccccccc}
 & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0
 \end{array} \\
 \hline
 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 0
 \end{array}$$


Booth Algorithm

- Since $0011110 = 0100000 - 0000010$, if we use the expression to the right, what will happen?

								0	1	0	1	1	0	1
								0	+1	0	0	0	-1	0
								0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	0	1	0	0	1	1	← 2's complement of the multiplicand
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	1	0	1	1	0	1						
0	0	0	0	0	0	0	0	0						
0	0	0	1	0	1	0	1	0	0	0	1	1	0	

Booth Algorithm

- In general, in the Booth scheme, -1 times the shifted multiplicand is selected when moving from 0 to 1, and +1 times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	0
																	
0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	0

Booth recoding of a multiplier.

Booth Algorithm

$$\begin{array}{r}
 01101 \quad (+13) \\
 \times 11010 \quad (-6) \\
 \hline
 \end{array}
 \quad \Rightarrow \quad
 \begin{array}{r}
 01101 \\
 0-1+1-10 \\
 \hline
 0000000000 \\
 111110011 \\
 00001101 \\
 1110011 \\
 000000 \\
 \hline
 1110110010 \quad (-78)
 \end{array}$$

Booth multiplication with a negative multiplier.

Booth Algorithm

Multiplier		Version of multiplicand selected by bit
Bit i	Bit $i-1$	
0	0	$0 \times M$
0	1	$+1 \times M$
1	0	$-1 \times M$
1	1	$0 \times M$


Booth multiplier recoding table.

Booth Algorithm

- Best case — a long string of 1's (skipping over 1s)
- Worst case — 0's and 1's are alternating

Worst-case multiplier


0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---



+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1
----	----	----	----	----	----	----	----	----	----	----	----	----	----	----	----

Ordinary multiplier


1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---



0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0
---	----	---	---	----	----	----	---	----	----	---	---	---	----	---	---

Good multiplier

0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1
---	---	---	---	---	---	---	---	---	---	---	---	---	---	---	---




0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1
---	---	---	----	---	---	---	---	----	---	---	---	----	---	---	----

Fast Multiplication

Bit-Pair Recoding of Multipliers

 - Bit-pair recoding halves the maximum number of summands (versions of the multiplicand).



(a) Example of bit-pair recoding derived from Booth recoding

Bit-Pair Recoding of Multipliers

Multiplier bit-pair		Multiplier bit on the right	Multiplicand selected at position
$i+1$	i	$i-1$	
0	0	0	0 X M
0	0	1	+1 X M
0	1	0	+1 X M
0	1	1	+2 X M
1	0	0	-2 X M
1	0	1	-1 X M
1	1	0	-1 X M
1	1	1	0 X M

(b) Table of multiplicand selection decisions

Bit-Pair Recoding of Multipliers

01101 (+13) X
11010 (-6)

$$\begin{array}{r}
 01101 \\
 0-1+1-10 \\
 \hline
 000000000 \\
 1111100011 \\
 00001101 \\
 1110011 \\
 000000 \\
 \hline
 1110110010 \quad (-78)
 \end{array}$$

Mul by -2 => add the number twice

-13= 10011

-13= 10011+

-26= 1 00110

$$\begin{array}{r}
 01101 \\
 0-1-2 \\
 \hline
 11111000110 \\
 111100011 \\
 000000 \\
 \hline
 1110110010
 \end{array}$$

solve using bit pair recoding

$$A = 010111 (+23)$$

$$B = 110110 (-10 \rightarrow 2\text{'s complement of } 110110)$$

Multiply the signed 2's complement numbers using the bit-pair recoding of the multiplier.

$$\begin{array}{r}
 \begin{array}{cccccc}
 & 0 & 1 & 0 & 1 & 1 & 1 \\
 \times & -1 & +2 & -2 & & & \\
 \hline
 111111 & 101 & 00 & 10 & & & \\
 00001 & 011 & 10 & & & & \\
 11101 & 001 & & & & & \\
 \hline
 11110 & 001 & 10 & 10 & & &
 \end{array}
 \end{array}$$

23
 $\times -10$ (Booth recoding 0 -1 +1 0 -1 0)
 $= -230$

Thus, the resultant value is $\boxed{-(230)}$.

$$\begin{array}{ccccccc}
 & & & & & & 0 \\
 & & & & & & \swarrow \\
 1 & 1 & 0 & 1 & 1 & 0 & \\
 \hline
 -1 & +2 & -2 & & & &
 \end{array}$$

$$\begin{array}{ccccccc}
 0 & -1 & +1 & 0 & -1 & 0 & \\
 \hline
 -2^0 & +2^1 & -2^1 & & & & \\
 -1 & +2 & -2 & & & &
 \end{array}$$

Consider the following binary numbers:

$$A = 110011 \quad (-13 \rightarrow 2\text{'s complement of } 110011)$$

$$B = 101100 \quad (-20 \rightarrow 2\text{'s complement of } 101100)$$


Multiply the signed 2's complement numbers using the bit-pair recoding of the multiplier.

$$\begin{array}{r}
 \begin{array}{cccccc} 1 & 1 & 0 & 0 & 1 & 1 \end{array} & -13 \\
 \times \begin{array}{cc} -1 & -1 \end{array} & \times -20 \text{ (Booth recoding } -1 \text{ } +1 \text{ } 0 \text{ } -1 \text{ } 0 \text{ } 0 \text{)} \\
 \hline
 00000000000000 & \\
 0000001101 & -2\text{'s complement} \\
 00001101 & \\
 \hline
 0001000000100 & = (+260)
 \end{array}$$

Thus, the resultant value is $\boxed{+(260)}$.


Carry-Save Addition of Summands

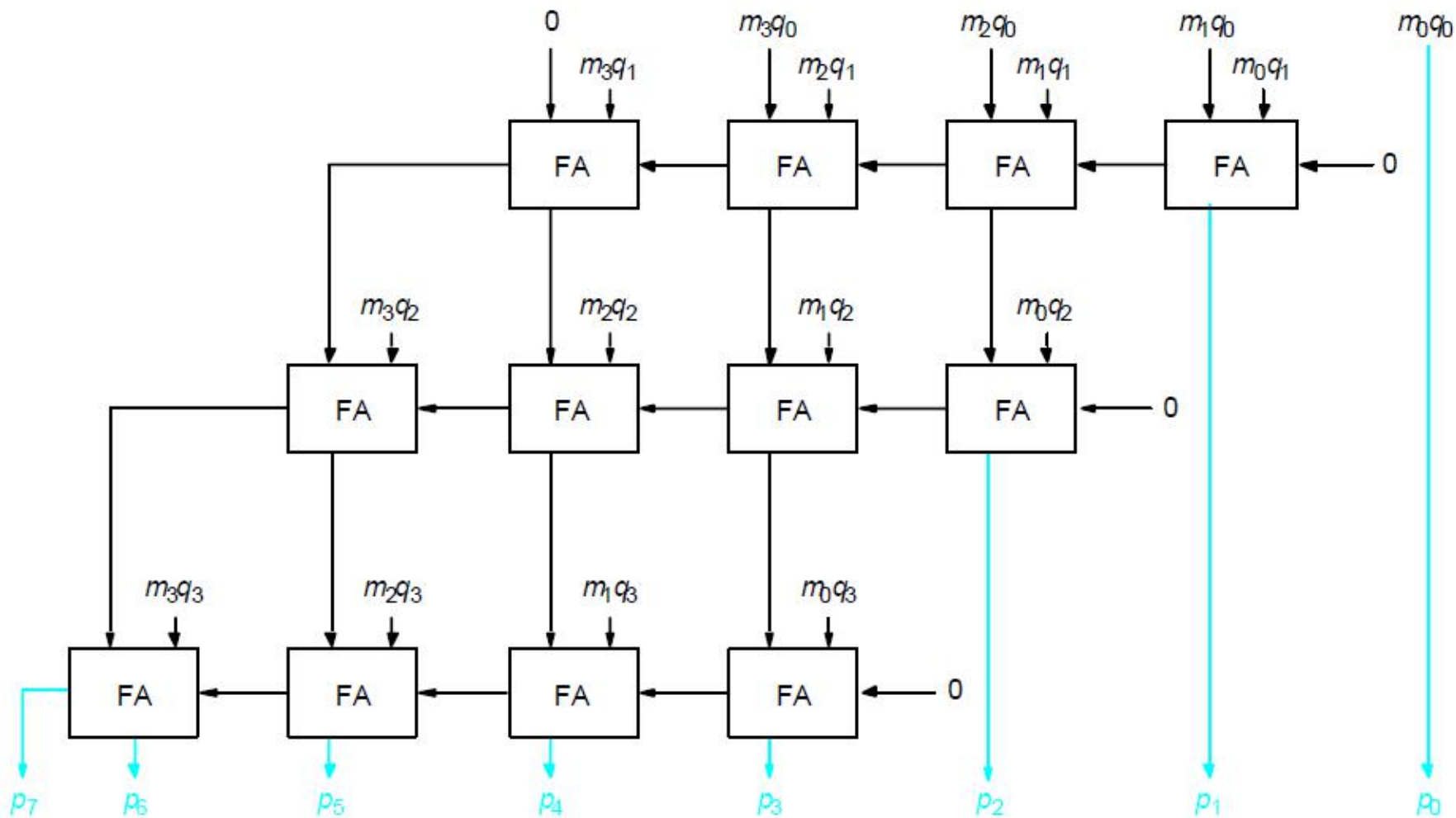- Carry save addition speeds up the addition process.
- In CSA, instead of letting the carries ripple along the rows, they can be saved and introduced into next row, at correct weighted positions.
- Consider the array for 4x4 multiplication
- First row consisting of just the AND gates that implement the bit products m_3q_0, m_2q_0, m_1q_0 and m_0q_0 .



Carry-Save Addition of Summands(Cont.,)

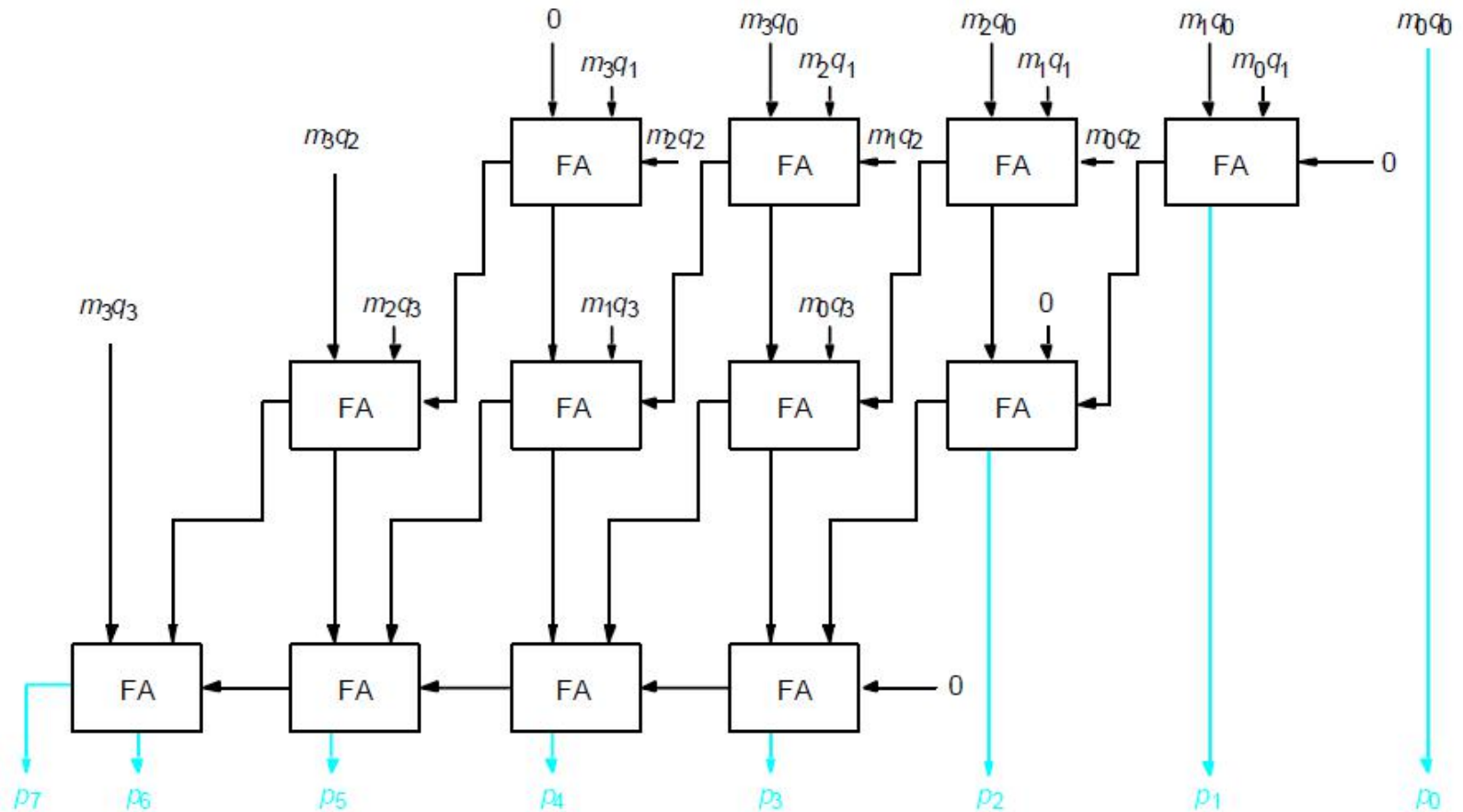- We see that carry from each stage ripples to the next stage delaying the PP terms
- Using CSA method, we can save carry and introduce them in the next row, at the correct weighted position
- This technique reduces the delay and frees up an input to the three full adders in the first row.



Two inputs of each full adder in the second row are the sum and carry outputs of the first row

Carry-Save Addition of Summands(Cont.,)

- Consider the addition of many summands, we can:
 - Group the summands in threes and perform carry-save addition on each of these groups in parallel to generate a set of S and C vectors in one full-adder delay
 - Group all of the S and C vectors into threes, and perform carry-save addition on them, generating a further set of S and C vectors in one more full-adder delay
 - Continue with this process until there are only two vectors remaining
 - They can be added in a RCA or CLA to produce the desired product

Carry-Save Addition of Summands

						1	0	1	1	0	1	(45)	M
					x	1	1	1	1	1	1	(63)	Q
						1	0	1	1	0	1	A	
				1		0	1	1	0	1		B	
			1	0		1	1	0	1			C	
		1	0	1		1	0	1				D	
	1	0	1	1		0	1					E	
1	0	1	1	0		1						F	
1	0	1	1	0	0	0	1	0	0	1	1	(2,835)	Product

Figure 6.17. A multiplication example used to illustrate carry-save addition as shown in Figure 6.18.

how to speed up?

- Using CSA principle, we can make group of three summands at a time , perform carry save addition in parallel using one full adder delay.(generates set of S and C)
- Group all generated S and C vectors in threes perform carry save addition on them to generate another set of S and C vector with one more FA delay.
- The process should continue until only two vectors remain to be added, which can be added in a carry lookahead adder to produce the desired product

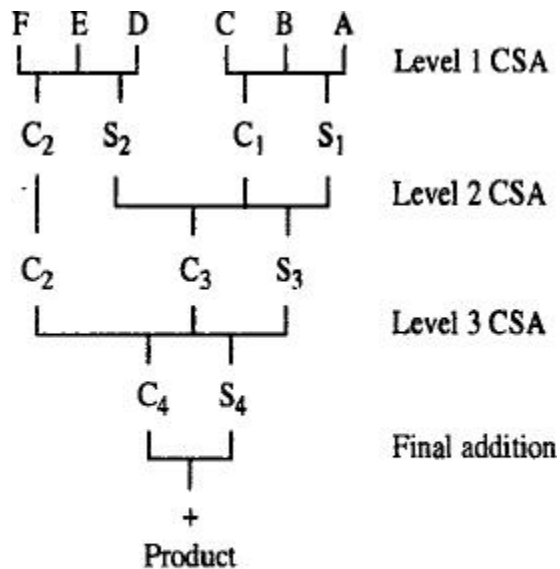


Figure 6.19 Schematic representation of the carry-save addition

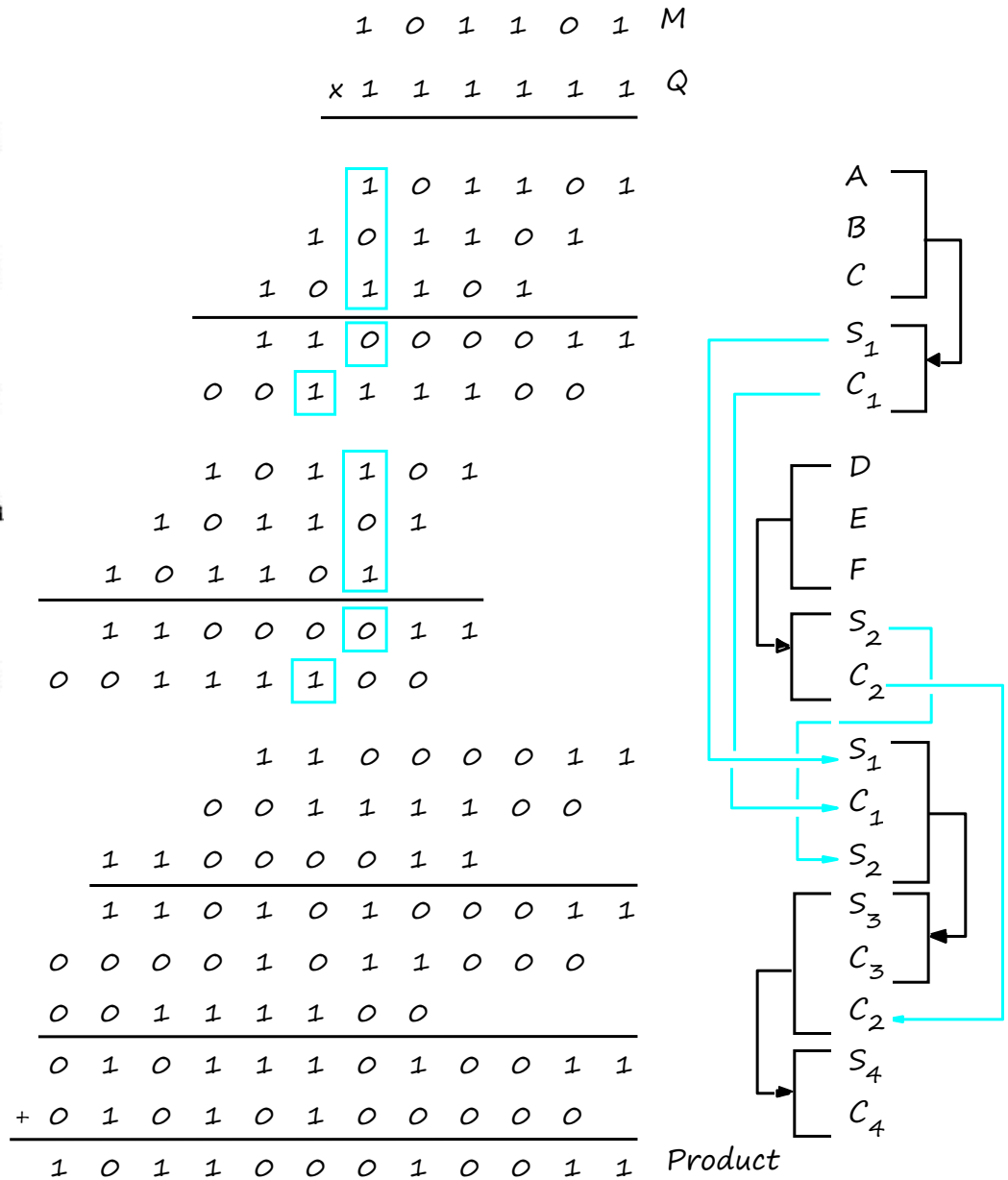


Figure 6.18.

The multiplication example from Figure 6.17 performed using carry-save addition.

Delay calculation

- Delay:
- 1 AND gate delay to generate all six summands at level 1
- 2 gate delays per CSA level till S4 and C4
=6 gate delays
- CLA gate delay =8
- Total delay for 6 bit number is $1+6+8=15$. If each gate delay is 10 ns, then CSA needs 150ns delay.
- array multiplier needs require $6(n-1)-1 = 29$ gate delay
- So When the number of summands is large, the time saved is proportionally much greater in CSA.

Integer Division

- Two methods:
Restoring &
Non restoring scheme

Restoring Division

I/P:

Register M is loaded with n-bit divisor (SIZE OF THE REGISTER IS $n+1$)

Register Q is loaded with n-bit dividend (size is n)

Register A is initially set to 0 (size $=n+1$)

O/P

The final quotient will be stored in n bit Q register.

The final remainder will be stored in n -bit "A" register.

Algorithm

1. Shift A and Q left one binary position
2. Subtract M from A, and place the answer back in A
3. If the sign of A is 1, set q_0 to 0 and add M back to A (restore A); otherwise, set q_0 to 1
4. Repeat these steps n times

Circuit Arrangement

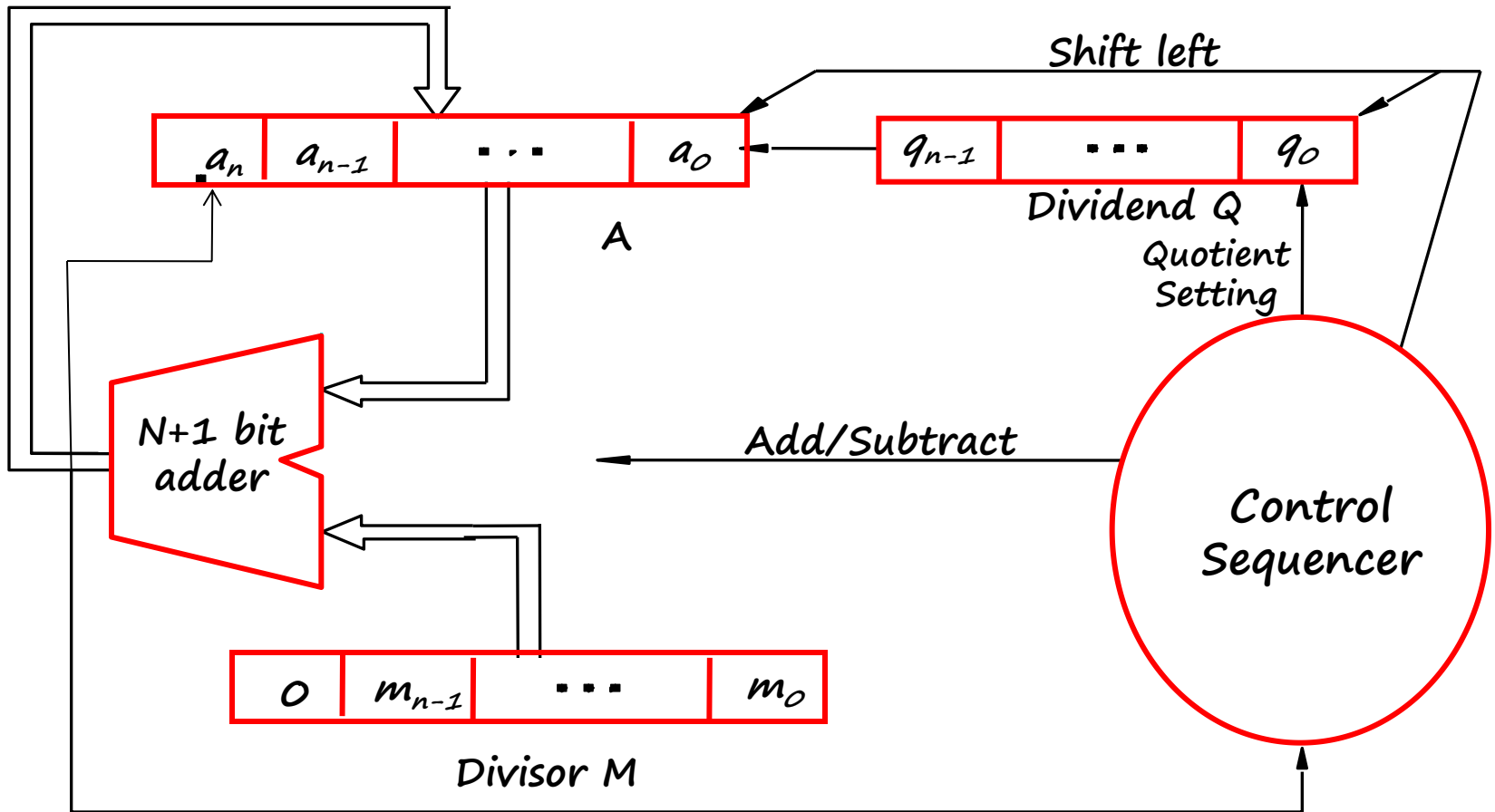


Figure 6.21. Circuit arrangement for binary division.

	A	Q	
Initially	0 0 0 0 0	1 0 0 0	First cycle
	0 0 0 1 1	M	
Shift	0 0 0 0 1	0 0 0 □	
Subtract	1 1 1 0 1		
Set q_0	1 1 1 1 0		Second cycle
Restore	1 1		
	0 0 0 0 1	0 0 0 0	
Shift	0 0 0 1 0	0 0 0 □	
Subtract	1 1 1 0 1		Third cycle
Set q_0	1 1 1 1 1		
Restore	1 1		
	0 0 0 1 0	0 0 0 0	
Shift	0 0 1 0 0	0 0 0 □	Fourth cycle
Subtract	1 1 1 0 1		
Set q_0	0 0 0 0 1		
Shift	0 0 0 1 0	0 0 0 1	
Subtract	1 1 1 0 1	0 0 1 □	
Set q_0	1 1 1 1 1		
Restore	1 1		
	0 0 0 1 0	0 0 1 0	
	Remainder	Quotient	

$$\begin{array}{r}
 10 \\
 11 \overline{) 1000} \\
 \underline{11} \\
 10
 \end{array}$$

Q
A

Nonrestoring Division

- Step 1: (Repeat n times)
 - If the sign of A is 0, shift A and Q left one bit position and subtract M from A ; otherwise, shift A and Q left and add M to A .
 - Now, if the sign of A is 0, set q_0 to 1; otherwise, set q_0 to 0.
- Step2: If the sign of A is 1, add M to A

A nonrestoring-division example.

$$\begin{array}{r} 10 \\ 11 \overline{) 1000} \\ \underline{11} \\ 10 \end{array}$$

Step 1:

Initially	0 0 0 0 0	1 0 0 0	} First cycle
Shift	0 0 0 0 1	0 0 0 	
Subtract	1 1 1 0 1		
Set q_0	1 1 1 1 0	0 0 0 0	} Second cycle
Shift	1 1 1 0 0	0 0 0 	
Add	0 0 0 1 1		
Set q_0	1 1 1 1 1	0 0 0 0	} Third cycle
Shift	1 1 1 1 0	0 0 0 	
Add	0 0 0 1 1		
Set q_0	0 0 0 0 1	0 0 0 1	} Fourth cycle
Shift	0 0 0 1 0	0 0 1 	
Subtract	1 1 1 0 1		
Set q_0	1 1 1 1 1	0 0 1 0	

Step 2:

Add	1 1 1 1 1	} Restore remainder
	0 0 0 1 1	
	0 0 0 1 0	
Remainder		

Quotient

Non restoring division example 11/5

		A	Q	
		0 0000	1011	
	M	00101		2's complement of 00101 11010 1's complement 1+ ----- 11011
Step 1	Shift Sub M Set q0	00001 11011 + ----- 1 1100	011- 0 11 0	1 st cycle
	Shift Add Set q0	11000 00101 ----- 1 1101	110- 1 1 00	2 nd cycle
	Shift Add Set q0	11011 00101 ----- 0 0000	100- 1 00 1	3 rd cycle
	Shift Sub M Set q0	00001 11011 ----- 1 1100	001- 0 01 0 Quotient	4 th cycle
Step 2	Restore	1 1100 00101 ----- 0 0001 Remainder		